

# ECE 4525: Project Report 2 + Bonus

Sergei Akhmatdinov  
Donovan Colo

December 8, 2021

# Contents

<b>1</b>	<b>Introduction</b>	<b>3</b>
<b>2</b>	<b>Design</b>	<b>3</b>
2.1	Finite State Machine Design .....	3
2.2	Hardware Design .....	4
2.3	Material Links .....	5
<b>3</b>	<b>Design Evaluation</b>	<b>6</b>
3.1	Simulations .....	6
<b>4</b>	<b>Conclusions</b>	<b>7</b>
<b>5</b>	<b>Team Contributions</b>	<b>8</b>
<b>6</b>	<b>Appendix</b>	<b>8</b>
6.1	FSM Design .....	8
6.2	Project .....	17

# 1 Introduction

In this project report, the design and evaluation of a peripheral I/O (PIO) chip will be discussed. The PIO chip represents a subset of an existing Intel i82C55A chip, with only a single peripheral port, a modified control and status register and only modes 0 and 1 supported. Using the datasheet of the original chip and the given specifications, asynchronous state machines were designed to replicate the chip functionality.

The chip functionality was then tested using the Xilinx Vivado simulator, by emulating a behaviour of an external peripheral device and a CPU controlling the peripheral ports and inputs and data ports and inputs respectively.

The base project covered mode 0 and mode 1 output only. Input functionality was added as part of the project bonus. For convenience, since the bonus project is a complete system and uses identical code to the base with added functionality, this report will cover the final version of the project, with bonus parts added.

It should be noted that due to time constraints, the VHDL code demonstrated in this report may differ from the VHDL code used in the final demonstration. This is because parts of the code may be modified to make the final design conform better to any initially misunderstood specifications and/or some changes may be made to improve existing functionality shortly after the submission of this report.

## 2 Design

### 2.1 Finite State Machine Design

Due to the lengthy process involved in asynchronous state machine design, the paper-and-pencil design process was moved to the Appendix.

The process that was demonstrated in class and used previously in the laboratory assessments was applied to design a rising and a falling edge detector, along with handshake interfaces used by mode 1 for the input and output functionality.

Mode 0 output was implemented as a listener for a rising edge of the ac-

tive low WR signal. Upon receiving a rising edge from WR, the contents of the data bus are either written to the peripheral device or to the control register, depending on the state of the A0 input.

Due to transparency requirements for the Mode 0 input, the interface reacts to the RD input being low to allow for the data bus to change while the pins on the peripheral inputs change.

Due to the short length of the pulse provided by the edge detectors, their state output was delayed using double inverters to lengthen the pulse.

Mode 1 handshake interface for the peripheral output works as follows: Initially, outputs OBF (Output Buffer Full) and INTR (Interrupt) are high. Input WR is then used to write data to the peripheral bus, using the same logic as Mode 0. A falling edge of WR clears the INTR output and a rising edge sets the OBF output. The system then waits for the peripheral device to acknowledge the output by pulsing the ACK input. Signals INTR and OBF are reset to their original states after a falling and a rising edge of ACK respectively. The whole process can then be repeated.


Mode 1 handshake interface for the peripheral input works as follows: Initially, outputs IBF (Input Buffer Full) and INTR (Interrupt) are low. The system waits to start input until a falling edge of the STB (Strobe) signal. The falling and rising edge of STB set signals IBF and INTR respectively. The system then waits to write the data to the data bus upon receiving a pulse of the RD signal, reacting to the falling edge of RD only to copy the data. The pulse of RD resets signals INTR on the falling edge and IBF on the rising edge. The whole process can then be repeated.

INTR output for modes 1 can be disabled by setting the control register bit 1 (INTE) to 0, in which case INTR will always be low.

## **2.2 Hardware Design**

A simplified schematic diagram of the module is provided below:

Figure 1: Schematic Diagram

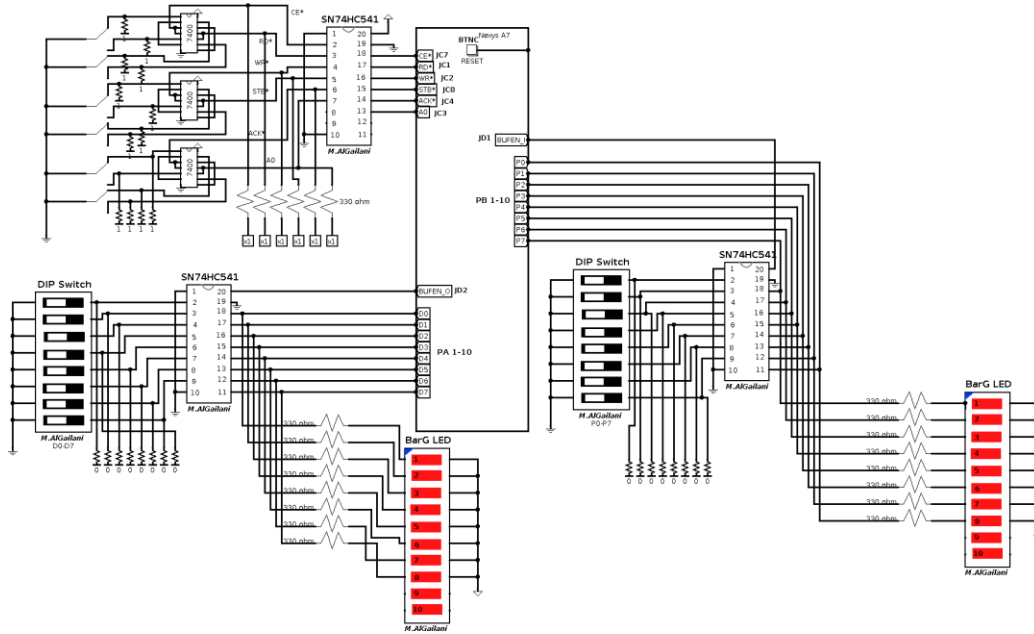

A 3-state setup was provided for the data and peripheral buses, with each input section protected by a non-inverting buffer. The input buffers are enabled only when input to the data or the peripheral buses is required.

3 quadruple NAND gate chips were used to provide bounce-free inputs CE, RD, WR, ACK, and A0. Although A0 was not required to be bounce free by the specifications, we decided that it was worth using an extra pair of NAND gates for the input. The RESET signal is represented by BTNC on the Nexys A7 board.

## 2.3 Material Links

Source materials used can be found in the appendix as follows:

- [Project Summary Report](#)
- [VHDL Source Code](#)
- [Rising Edge Detector](#)
- [Falling Edge Detector](#)


- Mode 1 Output State Machine Module
- Mode 1 Input State Machine Module
- Physical Constraints File
- Testing Stimuli

## 3 Design Evaluation

### 3.1 Simulations

Postroute simulations using the [testing stimuli](#) were first launched to test the design.

Figure 2: Postroute Simulations

 

Test steps were performed following the Demo Steps documents from the ECE 4525 website.

Since the design starts in mode 0 input (as per specs), it made sense to start testing the design from the bonus steps.

First, RD and CE relationship is checked. We make sure that the outputs remain in high impedance when CE = '1' or when RD and WR are both '0'. Then, we load the control register to mode 0 input. Nothing should change at this moment. Then, we attempt to input our data by writing 0x5a to the peripheral bus. At this moment, CE is 0, AO is 0 and RD is pulsed low. Upon detecting the falling edge of RD, the bits in the data bus should mirror those in the peripheral bus. The bits in the peripheral bus are then changed

to test transparency. When the bits on the peripheral bus are switched to 0x5c, the bits on the data bus are changed accordingly. But after the rising edge, D register is latched and changes in P do not affect the data bus any longer. This is demonstrated by setting the peripheral bus to 0xcc.

Afterwards, the control register is loaded to mode 1 input, with interrupt enabled. This is done by switching the least significant bits on the data bus to 111 or setting the data bus to 0x07, setting A0 to 1 and pulsing the WR input. We also set the peripheral bus to 0x69 to anticipate the input operation.

To check the status register, we set A0 to 1 and pulse RD. Once in mode 1, this would show 010. The most significant bit (3) is irrelevant when we are in input mode. We then send a strobe pulse (STB) that sets IBF and INTR high. Now, when we read the status register, we should read 111. We then pulse RD to write the peripheral to the data bus. This sets IBF and INTR to 0.

After testing the input, we write the control register to perform output. This is done by writing 000 to the control register.

In output mode, the data bus register contents are copied to the peripheral upon detecting a rising edge of WR when A0 = 0.

We test this functionality in mode 0 by writing 0x5a and 0xa5. The data is latched after every write.

Mode 1 output is then tested by writing 011 to the control register. 0x3c is written to the peripheral. Status register is checked at critical steps, such as before generating the write (WR) and acknowledge pulses.

The system is then reset to check reset to mode 0 input.

## **4 Conclusions**

The peripheral I/O chip performed as expected by the given specifications. Postroute simulations verified correct functionality, which was then further verified with hardware testing and demonstrations.

Asynchronous Finite State Machines for edge detection and handshaking interfaces were created using a pen-and-paper approach.

## **5 Team Contributions**

### **Sergei**

- FSM design
- VHDL Code
- Nexys A7 board hardware, P and D tri-state hardware and wiring
- Bonus Design
- This Report

### **Donovan**


- Project Schematic
- VHDL Code
- Bounce-free switch hardware and wiring
- Testing assistance
- Bonus Design

## **6 Appendix**

### **6.1 FSM Design**




## MODE 0 (BASIC OUTPUT)

 

231308-53

## MODE 1 (STROBED OUTPUT)

 

231308-55

Rising edge detector FSM

	WR	WR
	0	1
0	00	00
1	00	01

	0	1
0	0	0
1	0	1

 $Z = WR \text{ AND } Y_1$ 

Obviously free of essential hazards

	0	WR
0	1	0
1	1	0

 $Y_1 = \text{not } WR$ 

Needs some delay to increase pulse width, introduce double inverters

Mode 1 Out  
handshake

Outputs:  $int_R, obf$  Primitive state table

$st \backslash WR, Ack$	00	01	11	10
a	xx	b01	<u>a</u> 11	e11
b	f01	<u>b</u> 01	c00	xx
c	xx	b01	<u>c</u> 00	d01
d	f01	xx	a11	<u>d</u> 01
e	f01	xx	a11	<u>e</u> 11
f	<u>f</u> 01	b01	xx	e11

Implication table

	a	b	c	d	e
b	X				
c	X		✓		
d	X	X	X		
e	✓	X	X	X	
f	✓	✓	X	X	✓

(a b c d e f)

a: (aef) (bcd ef)

b: (bcf) (aef) (cdef)

c: (c) (bf) (bc) (aef) (def)

d: (d) (c) (bf) (bc) (aef) (ef)

e: (ef) (d) (c) (bf) (bc) (aef) (f)

	a	b	c	d	e	f
aef	*			*	*	
bf	*	*			*	
bc	*	*	*			
ef			*	*	*	
cd		*	*	*	*	
f				*		*

Selected stacks:


(aef) (bc) (d)

↓ ↓ ↓  
(a) (b) (d)

Reduced state table:

$st \backslash WR, Ack$	00	01	11	10
a	<u>a</u> 01	b01	<u>a</u> 11	<u>a</u> 11
b	a01	<u>b</u> 01	<u>b</u> 00	d01
d	a01	xx	a11	<u>d</u> 01

## Critical-race free assignment

 

	$y_1$				
$y_2$	<table border="1"> <tr> <td>a</td><td>b</td></tr> <tr> <td>d</td><td>z</td></tr> </table>	a	b	d	z
a	b				
d	z				

Requires transition state z

State coding:

	$y_1$	$y_2$
a	0	0
d	0	1
z	1	1
b	1	0

Assigned state table:

$s \backslash w, ack$	00	01	11	10
a	00	00/01	10/01	00/11
d	01	00/01	11/x	00/11
z	11	01/x	10/x	10/x
b	10	00/01	10/01	10/00

Check essential hazards:

Left side:

00  $\rightarrow$  10  $\rightarrow$  00  $\rightarrow$  10  
no hazards

Right side:


00  $\rightarrow$  00 no hazard

01  $\rightarrow$  00  $\rightarrow$  00  $\rightarrow$  00 delay  $y_2$


10  $\rightarrow$  01  $\rightarrow$  00  $\rightarrow$  00 delay  $y_1$

Both state vars delayed


K-maps + State & Output eqns (next page)

 

 
$$y_1 = \underline{(y_1 \cdot ACK)} + \underline{(\overline{WR} \cdot ACK)} + \underline{(y_1 \cdot \overline{y_2} \cdot WR)}$$


 
$$y_2 = \underline{(y_1 \cdot y_2 \cdot \overline{ACK})} + \underline{(y_1 \cdot WR \cdot \overline{ACK})} + \underline{(y_2 \cdot WR \cdot \overline{ACK})} + \underline{(\overline{y_1} \cdot y_2 \cdot \overline{WR} \cdot ACK)}$$


 
$$INTR = \underline{(\overline{y_1} \cdot \overline{y_2} \cdot WR)} + \underline{(\overline{y_1} \cdot WR \cdot \overline{ACK})}$$



$$DBF = \overline{y_1} + \overline{WR} + \overline{ACK}$$

Falling edge detector for Mode 0 input

		$\overline{RD}$	$\overline{RD}$
0	a	0	1
		1	0
1	b	0	0

		$RD$
		0
1	1	0
		0

$$Y_1 = \text{not } RD$$

		$RD$
		0
1	1	0
		0

$$Z = \text{not } RD \text{ AND not } Y_1$$

Introduce same delays as Mode 0 output

Mode 1 input

Primitive state table

out : ENTR, IBF

$s \setminus rd, ab$	00	01	11	10
a	xx	e00	a00	b01
b	f01	xx	c11	b01
c	xx	d01	a11	b01
d	f01	a01	a00	xx
e	f01	e00	a00	xx
f	a01	d01	xx	b01

# Implication table

b	X					
c	X	✓				
d	X	X	X			
e	✓	X	X	X		
f	X	✓	✓	✓	X	
	a	b	c	d	e	

(a b c d e f)

a: (a e) (b c d e f)

b: (b c f) (a e) (c d e f)

c: (c f) (b c f) (a e) (d e f)

d: (d f) (c f) (b c f) (a e) (e f)

e: (e) (d f) (c f) (b c f) (a e) (f)

		✓	✓		✓		✓
		↓	↓	✓	↓	✓	✓
		a	b	c	d	e	f
✓	b c f	*	*				*
✓	a e	*				*	
	c f		*				*
✓	d f			*			*
	e				*		
	f						*

Selected states:

(a e) (b c f) (d f)


(a e) (b c f) (d)

↓ ↓ ↓  
a b d

Reduced state table:

Critical-race free assignment:

$\begin{matrix} \text{Red} \\ \text{1/2B} \end{matrix}$	00	01	11	10
a	b 01	@ 00	@ 00	b 01
b	@ 01	d 01	@ 11	@ 01
d	b 01	@ 01	a 00	x x

 

	$y_1$	
	a	b
$y_2$	d	z

$y_1, y_2$   
a 00  
d 01  
z 11  
b 10

# Assigned state table

	$s \backslash \begin{matrix} RD \\ STB \end{matrix}$	00	01	11	10
a	00	10/01	00/00	00/00	10/01
d	01	11/01	00/01	00/00	11/x
z	11	10/01	01/01	10/11	10/x
b	10	00/01	11/01	00/11	00/01

		RD				
		1	0	0	1	a
		1	0	0	1	d
		1	0	1	1	z
$y_1$		1	1	1	1	b
		STB				

$$y_1 = \underline{1 \cdot \overline{STB}} + \underline{(y_1 \cdot RD)} + \underline{(y_1 \cdot \overline{y_2})}$$

		RD				
		0	0	0	0	a
		0	0	0	0	d
		0	1	0	0	z
$y_1$		0	1	0	0	b
		STB				

$$y_2 = \underline{(\overline{y_1} \cdot y_2 \cdot \overline{STB})} + \underline{(\overline{y_1} \cdot y_2 \cdot \overline{RD})} + \underline{(y_1 \cdot \overline{RD} \cdot STB)} + \underline{(y_2 \cdot \overline{RD} \cdot STB)}$$

Orange group fixes a static hazard

		RD				
		0	0	0	0	a
		0	0	0	x	d
		0	0	1	x	z
$y_1$		0	0	1	0	b
		STB				

$$INTR = \underline{(y_1 \cdot RD \cdot STB)}$$

		<u>RD</u>				
		1	0	0	1	a
		1	1	0	x	d
		1	1	1	x	z
y <sub>1</sub>		1	1	1	1	b
		<u>STB</u>				


A 4x5 grid with columns labeled RD and rows labeled a, d, z, b. The grid contains values 1, 0, x. A green loop encloses the first column (1, 1, 1, 1). A pink loop encloses the first two rows (1, 1) and (1, 1). A red loop encloses the last two rows (1, 1, 1, 1) and (1, 1, 1, 1). A vertical line labeled y<sub>1</sub> is to the left of the first column. A vertical line labeled y<sub>2</sub> is to the right of the last column.

$$IBF = \underline{(y_1)} + \underline{(\overline{STB})} + \underline{(y_2 \cdot \overline{RD})}$$



## 6.2 Project

Figure 3: Project Summary Report

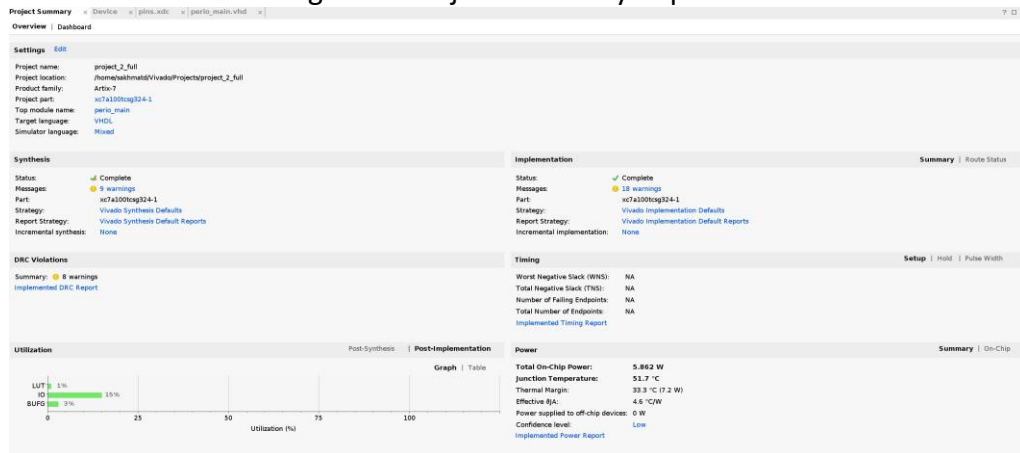

```
libraryIEEE; useIEEE.STD_LOGIC_1164.ALL;
```

```
entityperio_mainis
```

```
Port(
```

```
CE:instd_logic;
RD, WR:instd_logic;
A0:instd_logic;
RESET:instd_logic; ACK,
STB:instd_logic;
```

```
--
D:inoutstd_logic_vector(7downto0); P:inoutstd_logic_vector(7downto0);
```

```
--
BUFEN_I, BUFEN_O:outstd_logic;
```

```
--Debugsignals
```

```
MODE_LED, INTE_LED, INTR_LED, OBF_LED, IBF_LED, DIR_LED:
```

```
outstd_logic
```

```
);
```

```
endperio_main;
```

```
architectureBehavioralofperio_mainis
attributeDONT_TOUCH: string;
```

```

signal D_reg : std_logic_vector(7 downto 0) := (others => '0'); signal P_reg :
std_logic_vector(7 downto 0) := (others => '0'); signal MODE, INTE, TNTR :
std_logic := '0';
signal DIR : std_logic := '1'; signal OBF, IBF :
std_logic := '1';

--Prevent rising edge detectors from being optimized away
signal WR_RISE : std_logic := '0';
signal RD_FALL : std_logic := '0'; attribute DONT_TOUCH of WR_RISE : signal is "true";
attribute DONT_TOUCH of RD_FALL : signal is "true";

signal INTR_I, INTR_II, OBF_I, IBF_I : std_logic;
--signal Y1o, Y2o : std_logic;
--attribute DONT_TOUCH of Y1o, Y2o : signal is "true";

signal mode1i_enable, mode1o_enable : std_logic; component edge_detector
Port
(
    X : in std_logic;
    RISE : out std_logic
);
end component;
component fedge_detector Port
(
    X : in std_logic;
    FALL : out std_logic
);
end component;
component perio_mode1w
Port
(
    RESET, ENABLE : in std_logic; WR,
    ACK : in std_logic;
    INTR, OBF, Y1o, Y2o : out std_logic
);
end component;
component perio_mode1r
Port

```

```

        (
            ENABLE:instd_logic;
            RESET:instd_logic;
            RD, STB, A0:instd_logic;
            INTR, IBF, Y1o, Y2o:inoutstd_logic
        );
    endcomponent;

begin

    BUFEN_I <= '0' when ((RD = '0' or RD_FALL = '1') and CE = '0' and A0 = '0'
        and DIR = '1') else '1';
    BUFEN_O <= '0' when ((WR = '0' or WR_RISE = '1') and CE = '0') else '1';

    mode1i_enable <= DIR and MODE;
    mode1o_enable <= not DIR and MODE;

    mode1o: perio_mode1w
    portmap(
        ENABLE => mode1o_enable,
        RESET => RESET,
        WR => WR,
        ACK => ACK,
        INTR => INTR_I, OBF
        => OBF_I,
        Y1o => open,
        Y2o => open
    );

    mode1i: perio_mode1r
    portmap(
        ENABLE => mode1i_enable,
        RESET => RESET,
        RD => RD,
        STB => STB,
        A0 => A0,
        INTR => INTR_II, IBF
        => IBF_I,
        Y1o => open,
        Y2o => open
    );

    wr_edge: edge_detector portmap(

```

```

        X => WR,
        RISE => WR_RISE
    );
rd_edge: fedge_detector portmap(
    X => RD,
    FALL => RD_FALL
);
INTR <= INTR_I and INTE when (mode1o_enable = '1' and RESET = '0') else
    INTR_I and INTE when (mode1i_enable = '1' and RESET = '0') else '0';
INTR_LED <= INTR;
OBF <= OBF_I when (mode1o_enable = '1' and RESET = '0') else '1';
OBF_LED <= OBF;
IBF <= IBF_I when (mode1i_enable = '1' and RESET = '0') else '0';
IBF_LED <= IBF;

D <= (others => 'Z') when (CE = '1') else
    (0 => IBF, 1 => INTE, 2 => INTR, 3 => OBF, others => '0') when
    (MODE = '1' and RD = '0' and AO = '1') else
    P_reg when (DIR = '1') else
    (others => 'Z');

D_reg <= (others => '0') when (RESET = '1') else
    D when (WR_RISE = '1' and AO = '0' and CE = '0' and DIR = '0')
    else
    D_reg;

P_reg <= (others => '0') when (RESET = '1') else
    P when (RD_FALL = '1' and AO = '0' and CE = '0' and DIR = '1' and MODE = '1') else
    P when (RD = '0' and AO = '0' and CE = '0' and DIR = '1' and MODE
    = '0') else
    P_reg;

P <= (others => 'Z') when (CE = '1') else
    D_reg when (DIR = '0') else (others =>
    'Z');

```

```

--Controlregister

MODE <= '0' when (RESET = '1') else
    D(0) when (WR_RISE='1' and A0='1' and CE='0') else MODE;
MODE_LED <= MODE;

INTE <= '0' when (RESET = '1') else
    D(1) when (WR_RISE='1' and A0='1' and CE='0') else INTE;
INTE_LED <= INTE;

DIR <= '1' when (RESET = '1') else
    D(2) when (WR_RISE='1' and A0='1' and CE='0') else DIR;
DIR_LED <= DIR;
end Behavioral;

```

---

### Listing 1: Source Code

---

```

library IEEE; use IEEE.STD_LOGIC_1164.ALL;
entity edge_detector is Port
(
    X: in std_logic;
    RISE: out std_logic
);
end edge_detector;

architecture Behavioral of edge_detector is
    --This prevents the entire module from
    --being optimized away, from Xilinx Manual
    --
    https://www.xilinx.com/support/documentation/sw\_manuals/xilinx2012\_2/ug901-vivado-synthesis.pdf
    attribute DONT_TOUCH: string;
    signal Y1, delay1, delay2, delay3, delay4, delay5, delay6, delay7, delay8 : std_logic;
    attribute DONT_TOUCH of Y1, delay1, delay2, delay3, delay4, delay5,
    delay6, delay7, delay8: signal is "true";
begin
    --Add delay to lengthen the duration of

```

```

--thepulse
Y1 <=not(not(notX)); delay1
<=not(notY1); delay2
<=not(notdelay1); delay3
<=not(notdelay2); delay4
<=not(notdelay3); delay5
<=not(notdelay4); delay6
<=not(notdelay5); delay7
<=not(notdelay6); delay8
<=not(notdelay7); RISE <=
Xanddelay8;

endBehavioral;

```

---

## Listing 2: Rising Edge Detector

---

```

libraryIEEE; useIEEE.STD_LOGIC_1164.ALL;
entityfedge_detectoris Port
(
    X:instd_logic;
    FALL:outstd_logic
);
endfedge_detector;

architectureBehavioraloffedge_detectoris
    --Thispreventstheentiremodulefrom
    --beingoptimizedaway,fromXilinxManual
    --
    https://www.xilinx.com/support/documentation/sw\_manuals/xilinx2012\_2/ug901-vivado-synthesis.pdf
    attributeDONT_TOUCH: string;
    signalY1, delay1, delay2, delay3, delay4, delay5, delay6, delay7, delay8 : std_logic;
    attributeDONT_TOUCHofY1, delay1, delay2, delay3, delay4, delay5,
    delay6, delay7, delay8:signalis"true";
begin
    --Adddelaystolengththendurationof
    --thepulse
    Y1 <=not(not(notX)); delay1
    <=not(notY1); delay2
    <=not(notdelay1); delay3
    <=not(notdelay2);

```

```

delay4    <=not(notdelay3);
delay5    <=not(notdelay4);
delay6    <=not(notdelay5);
delay7    <=not(notdelay6);
delay8    <=not(notdelay7);
FALL<=notXandnotdelay8;

endBehavioral;

```

---

### Listing 3: Falling Edge Detector

---

```

libraryIEEE; useIEEE.STD_LOGIC_1164.ALL;
entityperio_mode1ris Port
(
    ENABLE:instd_logic;
    RESET:instd_logic;
    RD, STB, A0:instd_logic;
    INTR, IBF, Y1o, Y2o:inoutstd_logic
);
endperio_mode1r;
architectureBehavioralofperio_mode1ris signal y1,y2:
    std_logic:= '0';
begin
    --needtolatchstatesandoutputsifA0='1'toallow
    --forstatusregreading y1 <=
    ((notSTB)or
     (y1andRD)or (y1andnoty2))andnotRESETandENABLEwhen(A0
     ='0')
    else
        y1;
        y2 <= ((noty1andy2andnotSTB)or
               (noty1andy2andnotRD)or
               (y1andnotRDandSTB)or
               (y2andnotRDandSTB))andnotRESETandENABLEwhen(A0
        ='0')else
            y2;
        INTR<=y1andRDandSTBwhen(A0='0')else INTR;
    end
end

```

```

        IBF<=y1ornotSTBor(y2andnotRD)when(A0='0')else IBF;
endBehavioral;

```

---

#### Listing 4: Mode 1 Input

---

```

libraryIEEE; useIEEE.STD_LOGIC_1164.ALL;
entityperio_mode1wis
    Port
    (
        ENABLE:instd_logic;
        RESET:instd_logic; WR,
        ACK:instd_logic;
    );    INTR, OBF, Y1o, Y2o:outstd_logic
endperio_mode1w;

architectureBehavioralofperio_mode1wis
    --attributeDONT_TOUCH:string;
    signal y1,y2:std_logic:= '0';
    --attributeDONT_TOUCHof y1,y2:signalis"true";
begin

    --y1<=((ACKandY1)or
    --(notWRandACK)or
    --(WRandY1andnotY2))andnotRESETandENABLE;

    y1 <= ((y1andACK)or
        (notWRandACK)or
        (y1andnoty2andWR))andnotRESETandENABLE;

    --y2<=((WRandnotACKandY2)or
    --(notWRandY1andY2)or
    --(WRandnotACKandY1)or
    --(notWRandACKandnotY1andY2))andnotRESETand ENABLE;

    y2  <= ((y1andy2andnotACK)or
        (y1andWRandnotACK)or
        (y2andWRandnotACK)or

```



```

        (noty1andy2andnotWRandACK))andnotRESETand
ENABLE;
--INTR<=(WRandACKandnotY1)or(WRandnotY1andnotY2); INTR
<= (noty1andnoty2andWR)or(noty1andWRandACK);

OBF<=notY1ornotWRornotACK;

Y1o <= Y1;
Y2o <= Y2;
endBehavioral;

```

---

### Listing 5: Mode 1 Output

---

```

set_property ALLOW_COMBINATORIAL_LOOPS TRUE [get_nets D*] set_property
ALLOW_COMBINATORIAL_LOOPS TRUE [get_nets IBF*] set_property
ALLOW_COMBINATORIAL_LOOPS TRUE [get_nets OBF*] set_property
ALLOW_COMBINATORIAL_LOOPS TRUE [get_nets INTR_LED*]

# A0 gets registered as a clock
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets A0*]

set_property -dict { PACKAGE_PIN C17 IOSTANDARD LVCMOS33 } [get_ports { D[0] }];
#IO_L20N_T3_A19_15 Sch=ja[1]
set_property -dict { PACKAGE_PIN D18 IOSTANDARD LVCMOS33 } [get_ports { D[1] }];
#IO_L21N_T3_DQS_A18_15 Sch=ja[2]
set_property -dict { PACKAGE_PIN F18 IOSTANDARD LVCMOS33 } [get_ports { D[2] }];
#IO_L21P_T3_DQS_15 Sch=ja[3]
set_property -dict { PACKAGE_PIN G17 IOSTANDARD LVCMOS33 } [get_ports { D[3] }];
#IO_L18N_T2_A23_15 Sch=ja[4]
set_property -dict { PACKAGE_PIN D17 IOSTANDARD LVCMOS33 } [get_ports { D[4] }];
#IO_L16N_T2_A27_15 Sch=ja[7]
set_property -dict { PACKAGE_PIN E17 IOSTANDARD LVCMOS33 } [get_ports { D[5] }];
#IO_L16P_T2_A28_15 Sch=ja[8]
set_property -dict { PACKAGE_PIN F18 IOSTANDARD LVCMOS33 } [get_ports { D[6] }];
#IO_L22N_T3_A16_15 Sch=ja[9]
set_property -dict { PACKAGE_PIN G18 IOSTANDARD LVCMOS33 } [get_ports { D[7] }];
#IO_L22P_T3_A17_15 Sch=ja[10]

set_property -dict { PACKAGE_PIN D14 IOSTANDARD LVCMOS33 } [get_ports { P[0] }];
#IO_L1P_T0_ADOP_15 Sch=jb[1]
set_property -dict { PACKAGE_PIN F16 IOSTANDARD LVCMOS33 } [get_ports {

```

```

P[1] ]]; #IO_L14N_T2_SRCC_15 Sch=jb[2]
set_property -dict { PACKAGE_PIN G16 IOSTANDARD LVCMOS33 } [get_ports { P[2] }];
#IO_L13N_T2_MRCC_15 Sch=jb[3]
set_property -dict { PACKAGE_PIN H14 IOSTANDARD LVCMOS33 } [get_ports { P[3] }];
#IO_L15P_T2_DQS_15 Sch=jb[4]
set_property -dict { PACKAGE_PIN E16 IOSTANDARD LVCMOS33 } [get_ports { P[4] }];
#IO_L11N_T1_SRCC_15 Sch=jb[7]
set_property -dict { PACKAGE_PIN F13 IOSTANDARD LVCMOS33 } [get_ports { P[5] }];
#IO_L5P_T0_AD9P_15 Sch=jb[8]
set_property -dict { PACKAGE_PIN G13 IOSTANDARD LVCMOS33 } [get_ports { P[6] }];
#IO_0_15 Sch=jb[9]
set_property -dict { PACKAGE_PIN H16 IOSTANDARD LVCMOS33 } [get_ports { P[7] }];
#IO_L13P_T2_MRCC_15 Sch=jb[10]

set_property -dict { PACKAGE_PIN K1 IOSTANDARD LVCMOS33 } [get_ports { RD
    }]; #IO_L23N_T3_35 Sch=jc[1]
set_property -dict { PACKAGE_PIN F6 IOSTANDARD LVCMOS33 } [get_ports { WR
    }]; #IO_L19N_T3_VREF_35 Sch=jc[2]
set_property -dict { PACKAGE_PIN J2 IOSTANDARD LVCMOS33 } [get_ports { A0
    }]; #IO_L22N_T3_35 Sch=jc[3]
set_property -dict { PACKAGE_PIN G6 IOSTANDARD LVCMOS33 } [get_ports { ACK
    }]; #IO_L19P_T3_35 Sch=jc[4]
set_property -dict { PACKAGE_PIN E7 IOSTANDARD LVCMOS33 } [get_ports { CE
    }]; #IO_L6P_T0_35 Sch=jc[7]
set_property -dict { PACKAGE_PIN J3 IOSTANDARD LVCMOS33 } [get_ports { STB
    }]; #IO_L22P_T3_35 Sch=jc[8]

set_property -dict { PACKAGE_PIN N17 IOSTANDARD LVCMOS33 } [get_ports {
    RESET }]; #IO_L9P_T1_DQS_14 Sch=btnc
#set_property -dict { PACKAGE_PIN J4 IOSTANDARD LVCMOS33 } [get_ports { STB }];
#IO_L21P_T3_DQS_35 Sch=jc[9]
#set_property -dict { PACKAGE_PIN E6 IOSTANDARD LVCMOS33 } [get_ports { JC[10] }];
#IO_L5P_T0_AD13P_35 Sch=jc[10]

set_property -dict { PACKAGE_PIN H17 IOSTANDARD LVCMOS33 } [get_ports { MODE_LED }];
#IO_L18P_T2_A24_15 Sch=led[0]
set_property -dict { PACKAGE_PIN K15 IOSTANDARD LVCMOS33 } [get_ports { INTE_LED }];
#IO_L24P_T3_RS1_15 Sch=led[1]
set_property -dict { PACKAGE_PIN J13 IOSTANDARD LVCMOS33 } [get_ports { INTR_LED }];
#IO_L17N_T2_A25_15 Sch=led[2]
set_property -dict { PACKAGE_PIN N14 IOSTANDARD LVCMOS33 } [get_ports { OBF_LED }];
#IO_L8P_T1_D11_14 Sch=led[3]
set_property -dict { PACKAGE_PIN R18 IOSTANDARD LVCMOS33 } [get_ports { IBF_LED }];
#IO_L7P_T1_D09_14 Sch=led[4]

```

```

set_property -dict { PACKAGE_PIN V17 IOSTANDARD LVCMOS33 } [get_ports { DIR_LED }];
#IO_L18N_T2_A11_D27_14 Sch=led[5]

set_property -dict { PACKAGE_PIN H4 IOSTANDARD LVCMOS33 } [get_ports { BUFEN_I }];
#IO_L21N_T3_DQS_35 Sch=id[1]
set_property -dict { PACKAGE_PIN H1 IOSTANDARD LVCMOS33 } [get_ports { BUFEN_O }];
#IO_L17P_T2_35 Sch=id[2]

#set_property -dict { PACKAGE_PIN U17 IOSTANDARD LVCMOS33 } [get_ports { LED[6] }];
#IO_L17P_T2_A14_D30_14 Sch=led[6]
#set_property -dict { PACKAGE_PIN U16 IOSTANDARD LVCMOS33 } [get_ports { LED[7] }];
#IO_L18P_T2_A12_D28_14 Sch=led[7]
#set_property -dict { PACKAGE_PIN V16 IOSTANDARD LVCMOS33 } [get_ports { LED[8] }];
#IO_L16N_T2_A15_D31_14 Sch=led[8]
#set_property -dict { PACKAGE_PIN T15 IOSTANDARD LVCMOS33 } [get_ports { LED[9] }];
#IO_L14N_T2_SRCC_14 Sch=led[9]
#set_property -dict { PACKAGE_PIN U14 IOSTANDARD LVCMOS33 } [get_ports { LED[10] }];
#IO_L22P_T3_A05_D21_14 Sch=led[10]
#set_property -dict { PACKAGE_PIN T16 IOSTANDARD LVCMOS33 } [get_ports { LED[11] }];
#IO_L15N_T2_DQS_DOUT_CSO_B_14 Sch=led[11]
#set_property -dict { PACKAGE_PIN V15 IOSTANDARD LVCMOS33 } [get_ports { LED[12] }];
#IO_L16P_T2_CSI_B_14 Sch=led[12]
#set_property -dict { PACKAGE_PIN V14 IOSTANDARD LVCMOS33 } [get_ports { LED[13] }];
#IO_L22N_T3_A04_D20_14 Sch=led[13]
#set_property -dict { PACKAGE_PIN V12 IOSTANDARD LVCMOS33 } [get_ports { LED[14] }];
#IO_L20N_T3_A07_D23_14 Sch=led[14]
#set_property -dict { PACKAGE_PIN V11 IOSTANDARD LVCMOS33 } [get_ports { LED[15] }];
#IO_L21N_T3_DQS_A06_D22_14 Sch=led[15]

```

---

### Listing 6: Physical Constraints

---

```

restart

add_force STB 1
add_force ACK 1
add_force CE 1
add_force A0 1
add_force RD 1
add_force WR 1
add_force RESET 1 run
100ns

```

```

add_force RD 0
add_force RESET 0

run 50ns

add_force RD 1
add_force CE 0
run 50ns
add_force -radix hex D 0x04 add_force
WR 0
run 50ns
add_force WR 1
run 10ns
remove_force D
run 50ns

add_force -radix hex P 0x5a
add_force AO 0
add_force RD 0

run 50 ns
add_force -radix hex P 0x5c run
50ns
add_force RD 1
run 10ns
add_force -radix hex P 0xcc

run 50ns
add_force -radix hex D 0x07
add_force AO 1
add_force WR 0

run 50ns
add_force WR 1
run 10ns
remove_force D
run 50ns

```

```

add_force RD 0
run 50ns
add_force RD 1

add_force -radix hex P 0x69
add_force A0 0
add_force STB 0
run 50ns
add_force STB 1
run 50ns

add_force A0 1
run 10ns
add_force RD 0
run 50ns
add_force RD 1
run 50ns

add_force A0 0
add_force RD 0
run 50ns

add_force RD 1
run 10ns
remove_force P
run 50ns

puts "Output"

add_force -radix hex D 0x00 add_force
A0 1
add_force WR 0
run 50ns
add_force WR 1
run 10ns
remove_force D
run 50ns

add_force A0 0
add_force -radix hex D 0x5a
add_force WR 0
run 50ns
add_force WR 1
run 10ns

```

```

remove_force D
run 50ns

add_force -radix hex D 0xa5 add_force
WR 0
run 50ns
add_force WR 1
run 10ns
remove_force D
run 50ns

add_force A0 1
add_force -radix hex D 0x03
add_force WR 0
run 50ns
add_force WR 1
run 10ns
remove_force D
run 50ns

add_force RD 0
run 50ns
add_force RD 1
run 50ns

add_force A0 0
add_force -radix hex D 0x3c
add_force WR 0
run 50ns
add_force WR 1
run 10ns
remove_force D

add_force A0 1
add_force RD 0
run 50ns
add_force RD 1
run 50ns

add_force ACK 0
run 50ns
add_force ACK 1
run 50ns

add_force RD 0

```

```
run 50ns
add_force RD 1
run 50ns

add_force A0 0
add_force -radix hex D 0xc3
add_force WR 0
run 50ns
add_force WR 1
run 10ns
remove_force D

add_force RESET 1
run 50ns add_force
RESET 0 run 50ns
```

---

Listing 7: Testing File